

DIGITAL LOGIC WORKED EXAMPLE: SCHEMATIC TO FUNCTION*

Kiran Pathakota
Ayana Andalcio

This work is produced by OpenStax-CNX and licensed under the
Creative Commons Attribution License 3.0[†]

Abstract

This is a worked example demonstrating how to obtain the function from a given transistor level schematic.

In the following exercise, a transistor level schematic will be analyzed and its underlying function will be found.

Exercise 1: Schematic to Function

(Solution on p. 3.)

Fill out the truth table for the following mystery schematic (Fig 1) and determine the function.

*Version 1.1: Dec 16, 2010 12:44 pm -0600

[†]<http://creativecommons.org/licenses/by/3.0/>

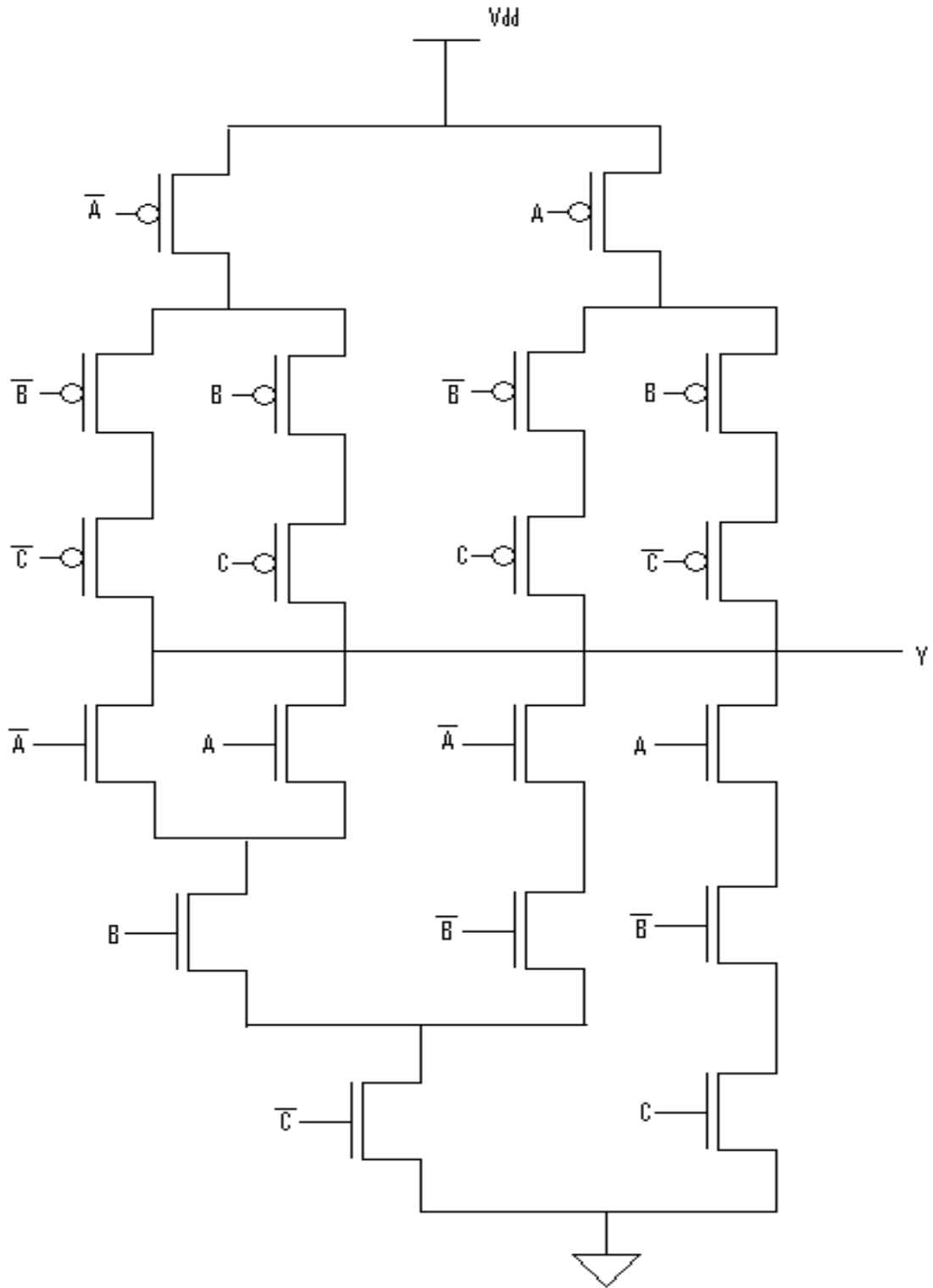


Figure 1

Solutions to Exercises in this Module

Solution to Exercise (p. 1)

Working It Out

Step 1: States of a transistor

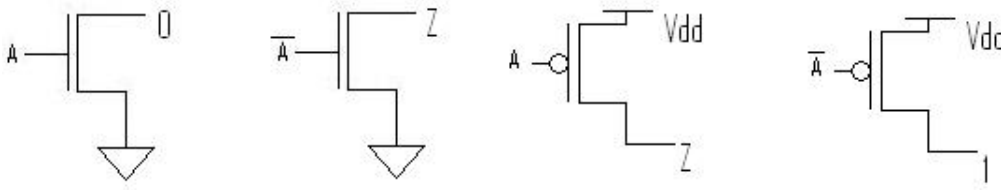


Figure 2: Consider A to be high (1)

Note that this is a valid schematic and that the p-MOS transistors are connected to the ground and the n-MOS transistors are connected to Vdd

Step 2: Truth Table

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Figure 3

Step 3: Complete the truth table with the corresponding output Y to its input

Truth Table

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Figure 4

Step 4: $Y = A'B'C + A'BC' + AB'C' + ABC$ OR $Y = (A' + B' + C')(A' + B + C)(A + B' + C')(A + B + C')$

Step 5: Also, try to notice patterns that you have already learned about. Clearly, the output is high only when there is an odd number of inputs high. Thus, we can conclude that this is a 3 - input XOR.

Answer: $Y = \text{XOR}(A, B, C)$